
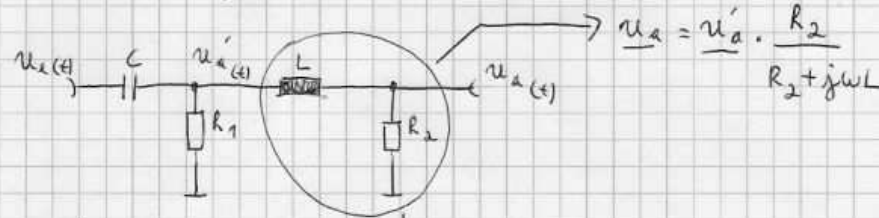


[ Teil 1 ]

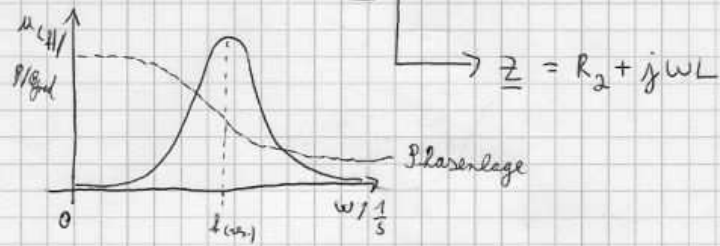Übertragungsfunktion Bandpass - Herleitung!



$$\underline{u}_a = \underline{u}_a' \cdot \frac{R_2}{R_2 + j\omega L}$$



$$H(j\omega) = \frac{\underline{u}_a'}{\underline{u}_x} = \frac{R_1 \cdot (R_2 + j\omega L)}{R_1 + R_2 + j\omega L} \quad | \cdot j\omega C \cdot (R_1 + R_2 + j\omega L)$$

$$\frac{1}{j\omega C} + \frac{R_1(R_2 + j\omega L)}{R_1 + R_2 + j\omega L} \quad | \cdot j\omega C \cdot (R_1 + R_2 + j\omega L)$$

$$\underline{u}_a' = \underline{u}_x \cdot \frac{R_1(R_2 + j\omega L) \cdot j\omega C \cdot (R_1 + R_2 + j\omega L)}{(R_1 + R_2 + j\omega L)}$$

$$\frac{R_1 + R_2 + j\omega L + R_1(R_2 + j\omega L) \cdot j\omega C (R_1 + R_2 + j\omega L)}{(R_1 + R_2 + j\omega L)}$$

$$= \underline{u}_x \cdot \frac{j\omega R_1 C (R_2 + j\omega L)}{R_1 + R_2 + j\omega L + j\omega R_1 C (R_2 + j\omega L)}$$

$$= \underline{u}_x \cdot \frac{j\omega R_1 R_2 C - \omega^2 R_1 L C}{R_1 + R_2 + j\omega L + j\omega R_1 R_2 C - \omega^2 R_1 L C} \cdot \frac{R_2}{R_2 + j\omega L}$$

## [Teil 2]

## Übertragungsfunktion Bandpass

- Teil 2 -

$$\begin{aligned} \frac{u_a}{u_e} &= \frac{j\omega R_1 R_2^2 C - \omega^2 R_1 R_2 L C}{R_2 (R_1 + R_2) + j\omega R_2 L + j\omega R_1 R_2^2 C - \omega^2 R_1 R_2 L C + j\omega (R_1 + R_2) L - \omega^2 L^2 - \omega^2 R_1 R_2 L C - j\omega^3 R_1 L^2 C} \\ &= \frac{j\omega R_1 R_2^2 C - \omega^2 R_1 R_2 L C}{[R_2 (R_1 + R_2) - 2\omega^2 R_1 R_2 L C - \omega^2 L^2] + j[\omega R_2 L + \omega R_1 R_2^2 C + \omega (R_1 + R_2) L - \omega^3 R_1 L^2 C]} \\ &= \frac{j\omega R_1 R_2^2 C - \omega^2 R_1 R_2 L C}{[R_2 (R_1 + R_2) - \omega^2 (L^2 + 2R_1 R_2 L C)] + j[\omega (R_1 R_2^2 C + \underbrace{(R_1 + R_2) L + R_2 L}_{\rightarrow R_1 L + 2R_2 L}) - \omega^3 R_1 L^2 C]} \end{aligned}$$

Normalform  
Gesamtausdruck - Eulersche Form:

$$\frac{u_a}{u_e} = \frac{\omega^2 R_1 R_2 L C - j\omega R_1 R_2^2 C}{[\omega^2 (L^2 + 2R_1 R_2 L C) - R_2 (R_1 + R_2)] - j[\omega (R_1 R_2^2 C + (R_1 + R_2) L + R_2 L) - \omega^3 R_1 L^2 C]}$$

Gesamtausdruck - Eulersche Form:

$$\frac{u_a}{u_e} = \frac{\sqrt{(\omega^2 R_1 R_2 L C)^2 + (\omega R_1 R_2^2 C)^2}}{\sqrt{[\omega^2 (L^2 + 2R_1 R_2 L C) - R_2 (R_1 + R_2)]^2 + [\omega (R_1 R_2^2 C + R_1 L + 2R_2 L) - \omega^3 R_1 L^2 C]^2}} \cdot e^{j\varphi}$$

→ siehe nächste Seite!

[Teil 3]

Übertragungsfunktion Bandpass

$$\| \varphi = \varphi_{\text{Zähler}} - \varphi_{\text{Nenner}} \|$$

$$\tan \varphi_1 = - \frac{\omega^2 R_1 R_2^2 C}{\omega^2 R_1 R_2 L C} = - \frac{R_2}{\omega L} \quad ; \quad \tan \varphi_2 = - \frac{\omega (R_1 R_2^2 C + R_1 L + 2 R_2 L - \omega^3 R_1 L^2 C)}{\omega^2 (L^2 + 2 R_1 R_2 L C) - R_2 (R_1 + R_2)}$$

$$\Rightarrow \varphi = \arctan \left( - \frac{R_2}{\omega L} \right) - \arctan \left[ - \frac{\omega (R_1 R_2^2 C + R_1 L + 2 R_2 L - \omega^3 R_1 L^2 C)}{\omega^2 (L^2 + 2 R_1 R_2 L C) - R_2 (R_1 + R_2)} \right]$$

$$\Rightarrow \varphi = 0^\circ \text{ setzen!}$$

$$\frac{R_2}{\omega L} = \frac{\omega (R_1 R_2^2 C + R_1 L + 2 R_2 L - \omega^3 R_1 L^2 C)}{\omega^2 (L^2 + 2 R_1 R_2 L C) - R_2 (R_1 + R_2)}$$

$$\Rightarrow \frac{R_2}{\omega L} [\omega^2 (L^2 + 2 R_1 R_2 L C) - R_2 (R_1 + R_2)] = \omega (R_1 R_2^2 C + R_1 L + 2 R_2 L) - \omega^3 R_1 L^2 C$$

$$R_2 \omega L + 2 \omega R_1 R_2^2 C - \frac{R_2^2}{\omega L} (R_1 + R_2) = \omega R_1 R_2^2 C + \omega R_1 L + 2 \omega R_2 L - \omega^3 R_1 L^2 C \quad | \cdot \omega L$$

[Teil 4]

Übertragungsfunktion Bandpass

$$R_2 \omega^2 L^2 + 2 \omega^2 R_1 R_2^2 LC - R_2^2 (R_1 + R_2) = \omega^2 R_1 R_2^2 LC + \omega^2 R_1 L + 2 \omega^2 R_2 L^2 - \omega^4 R_1 L^3 C$$

$$\omega^4 R_1 L^3 C + 2 \omega^2 R_1 R_2^2 LC - \omega^2 R_1 R_2^2 LC + R_2 \omega^2 L^2 - 2 R_2 \omega^2 L^2 - \omega^2 R_1 L^2 - R_2^2 (R_1 + R_2) = 0$$

$$\Rightarrow \omega^4 R_1 L^3 C + \omega^2 R_1 R_2^2 LC - R_2 \omega^2 L^2 - \omega^2 R_1 L^2 - R_2^2 (R_1 + R_2) = 0$$

$$\omega^4 + \omega^2 \frac{R_1 R_2^2 \cancel{LC}}{R_1 L^3 \cancel{C}} - \frac{R_2 \omega^2 \cancel{L^2}}{R_1 L^3 \cancel{C}} - \omega^2 \frac{\cancel{R_1 L^2}}{R_1 L^3 \cancel{C}} - \frac{R_2^2}{R_1 L^3 C} (R_1 + R_2) = 0$$

$$\omega^4 + \left( \frac{R_2^2}{L^2} - \frac{R_2}{R_1} \cdot \frac{1}{LC} - \frac{1}{LC} \right) \omega^2 - \frac{R_2^2}{L^3 C} - \frac{R_2^3}{R_1 L^3 C} = 0$$

$$\Rightarrow \omega^2 = x \text{ setzen!}$$

$$x^2 + \left( \frac{R_2}{L^2} - \frac{1}{LC} \left( \frac{R_2}{R_1} + 1 \right) \right) x - \frac{R_2^2}{L^3 C} \left( \frac{R_2}{R_1} + 1 \right) = 0$$

[Teil 5]

Übertragungsfunktion Bandpass

$$\Rightarrow x_{1/2} = \frac{-\left(\frac{R_2}{L^2} - \frac{1}{LC} \left(\frac{R_2}{R_1} + 1\right)\right) \pm \sqrt{\left(\frac{R_2}{L^2} - \frac{1}{LC} \left(\frac{R_2}{R_1} + 1\right)\right)^2 + \frac{R_2^2}{L^3 C} \left(\frac{R_2}{R_1} + 1\right)}}{2}$$

$$\Rightarrow f_{res.} = \frac{\sqrt{x}}{2\pi} = \frac{\sqrt{\omega^2}}{2\pi} = \frac{\omega}{2\pi} //$$